



Date: 05-04-2019

Dept. No.

Max. : 100 Marks

Time: 01:00-04:00

**Section – A**

Answer **ALL** the Questions

**(10 \* 2 = 20 Marks)**

- 1) Draw the symbol & truth table for NOR gate.
- 2) What is called Excitation Table?
- 3) What do you mean by Encoder?
- 4) What is called Registers?
- 5) What is effective address?
- 6) What is called Program Counter?
- 7) What is the use of INC instruction?
- 8) Write the microoperations to add the element to the accumulator.
- 9) List any four Zero address instruction.
- 10) What is called control word?

**Section – B**

Answer any **FIVE** questions

**(5 \* 8 = 40 Marks)**

- 11 Explain the block diagram of Digital Computer.

**(OR)**

Simplify the Boolean expression by using Karnaugh map  $F(A,B,C) = (0,2,4,5,6)$

- 12 What is Decoder? Explain how the 3X8 decoder is implemented.

**(OR)**

Explain in detail about the working of Multiplexer.

- 13) Explain about the various types of computer Instruction Formats.

**(OR)**

Explain the various types of registers used in Basic computer.

- 14). Explain in detail about the different phases involved in Instruction cycle with a neat flowchart.

**(OR)**

With a neat flowchart, explain about the Interrupt cycle.

- 15) Discuss the different fields involved in Instruction Formats.

**(OR)**

Explain in detail about the different types of address instructions with an example.

**Section - C**

Answer any **TWO** questions

**(2 \* 20 = 40 Marks)**

16) i) Explain in detail about the Full adder circuit with a neat diagram. **(10 Marks)**

ii) What is Flipflop? Explain the working of D Flip flop. **(10 Marks)**

17) i) What is Shift Register? Explain about how the register will capable of shifting its data in both directions. **(10 Marks)**

ii) Discuss the different types of instruction present in Instruction Formats. **(10 Marks)**

18) Explain in detail about the Addressing modes with an example

★★★★★★