# LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034



### **B.C.A.**DEGREE EXAMINATION - **COMPUTER APPLICATIONS**

### SECOND SEMESTER - APRIL 2019

#### CA 2505- DIGITAL LOGIC FUNDAMENTALS

Date: 04-04-2019 Dept. No		Max. : 100 Marks
---------------------------	--	------------------

Time: 09:00-12:00

#### PART - A

# **ANSWER ALL QUESTIONS**

 $(10 \times 2 = 20 \text{ marks})$ 

- 1. Convert (0.6875)10 to binary.
- 2. Implement AND gate using NOR gates.
- 3. Give the truth table for half adder and write the expression for sum and carry.
- 4. What is EPROM?
- 5. What is the operation of JK flip flop?
- 6. Write any two applications of shift registers.
- 7. What do you mean by indirect address?
- 8. Define Operation code.
- 9. What is non-volatile memory?
- 10. What do you mean by addressing modes?

#### PART - B

# **ANSWER ALL QUESTIONS**

 $(5 \times 8 = 40 \text{ marks})$ 

11.a) Simplify the following expressions in (1) sum of products and (2) product ofsums

i) 
$$AC' + B'D + A'CD + ABCD$$
 (4)

$$ii)(A' + B' + D') (A+B'+C') (A'+B+D') (B+C'+D') (4)$$

(Or)

- b) i)Convert (126)10 to Octal number and binary number. (4)
  - ii)Find the Octal equivalent of the hexadecimal number DC.BA. (2)
  - iii)Find the octal equivalent of hexadecimal numbers AB.CD (2)
- 12. a) Design and explain about full adder with neat diagram.(8)

(Or)

b) Design a full subtractor and derive expression for difference and borrow.(8)

13.a) Explain in detail about counters.

(Or)

- b) Explain the operation of a JK Master Slave flip flop with logic diagram. (8)
- 14.a) Explain in detail about the common bus system of a processor with neat Diagram.(8)

  (Or)
- b) Discuss in detail about the stored program architecture of computer system with neat diagram.(8)
- 15. a) Explain in detail about various addressing modes with suitable example.(8)

(Or)

b) Explain in detail about types of computer instructions. Give examples.(8)

## PART - C

## **ANSWER ANY TWO QUESTIONS**

 $(2 \times 20 = 40 \text{ marks})$ 

16. a) Simplify the given Boolean function in POS form using K-map (10)

$$F(A,B,C,D) = m(0,1,4,7,8,10,12,15)+d(2,6,11,14)$$

- b) Explain in detail about multiplexers.(10)
- 17. a) Explain in detail about RS flip flop with suitable diagram.(10)
  - b) Explain about various registers of computer system.(10)
- 18. a)Explain about instruction formats with examples. (10)
  - b) What is ROM? Explain in detail about its types.(10)

