

# LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034



**B.Sc. DEGREE EXAMINATION – COMPUTER SCIENCE**

**THIRD SEMESTER – APRIL 2016**

**PH 3106 – APPLIED ELECTRONICS**

Date: 06-05-2016

Dept. No.

Max. : 100 Marks

Time: 09:00-12:00

## PART A

ANSWER ALL QUESTIONS

(10×2=20)

1. What is Fermi level?
2. Define CMRR.
3. Write four important characteristics of an ideal operational amplifier.
4. What is a semiconductor? How is it classified?
5. What is a multiplexer?
6. State Demorgan's theorem.
7. What is a Flip flop?
8. Draw the block diagram of a T Flip Flop using JK Flip Flop and give its truth table.
9. State the different types of computer registers?
10. What is a cache memory?

## PART B

ANSWER ANY FOUR QUESTIONS

(4×7.5=30)

11. Write short notes on (a) intrinsic semiconductors (b) Zener diode.
12. Explain the working of an OP-AMP non inverting amplifier with a circuit diagram.
13. Explain how NOR is used as universal building block with neat diagrams.
14. With a neat diagram and truth table discuss the working of a Shift counter.
15. Draw the block diagram and the memory hierarchy in a computer system.

## PART C

ANSWER ANY FOUR QUESTIONS

(4×12.5=50)

16. Describe the operation of a NPN Transistor in common emitter mode.
17. Explain with circuit diagram, the working of an op-amp based 4 bit R-2R ladder D/A converter.
18. (a) Simplify using K – map  $Y=F(A,B,C,D)=\Sigma(0,1,4,5,10,11,14,15)$ . (8.5marks)  
(b) Explain the working of a 4 input multiplexer. Give its logic circuit and output. (4 marks)
19. Explain the working of JK Flip flop with a neat diagram.
20. (a) Explain various types of ROM. (6 marks)  
(b) Explain the working of a full adder with circuit diagram and truth table. (6.5marks)

\*\*\*\*\*