



Date: 07-05-2018
Time: 09:00-12:00

Dept. No.

Max. : 100 Marks

PART- A

Answer All Questions

(10×2=20 marks)

1. Define constant current source.
2. State the superposition theorem.
3. What is a DC load line?
4. What is a multivibrator?
5. Mention any four characteristics of an ideal op-amp?
6. Explain the action of an op-amp as a non-inverting amplifier.
7. Draw the logic symbol and truth table of D-flip-flop.
8. What is a shift register?
9. Mention any two advantages of integrated circuits.
10. What is VLSI?


PART -B

Answer Any FOUR Questions:

(4×7.5=30 marks)

11. State Norton's theorem, find the current through the $8\ \Omega$ resistor in the given network by using Norton's theorem.

$4\ \Omega$ $5\ \Omega$

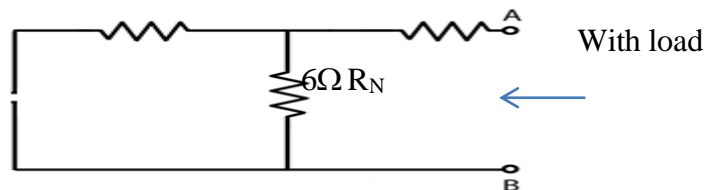

12. With a neat circuit diagram, discuss the action of a RC coupled amplifier. Discuss the frequency response curve.
13. Explain how an op-amp can be used as a difference amplifier and, obtain an expression for the output.
14. Describe the working of a RS-Flip Flop.
15. How will you make a monolithic IC?
16. Explain the working of a Colpitt's oscillator with a neat circuit diagram.

PART -C

Answer Any FOUR Questions

(4×12.5=50 marks)

17.State and explain thevenin theorem.

18.Describe the construction and working of an astablemultivibrator with its wave form.

19.Describe the construction and working of JFET.

20. Explain the function of 4-bit ripple counter with necessary diagram, truth table and wave form.

21.Explain how (i) a diode (ii) a transistor (iii) a resistor and (iv) a capacitor can be fabricated on a monolithic.

22.With a neat circuit diagram and truth table describe the operation of a J-K Master Slave flip flop.
