



**LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034**

**B.Sc. DEGREE EXAMINATION – PHYSICS**

**FIFTH SEMESTER – APRIL 2018**

**PH 5404/PH 5401 – ELECTRONICS - II**

Date: 08-05-2018  
Time: 09:00-12:00

Dept. No.

Max. : 100 Marks

**PART A**

Answer **ALL** the Questions

(10 × 2 = 20)

1. Give two characteristics of an ideal op-amp.
2. Calculate the voltage gain of an inverting amplifier with feedback resistance of 20 KΩ and input resistance of 2 KΩ.
3. Define the terms i) Resolution and ii) linearity of A/D converter.
4. What is the disadvantage in parallel A/D converter?
5. Write the difference between SSI and VLSI chips.
6. What is linear and non-linear IC?
7. What is the function of a program counter?
8. Differentiate between SUB B and CMP B instructions.
9. Write an assembly language program to add two 8 bit numbers.
10. What is meant by subroutine in μP 8085?

**PART B**

Answer any **FOUR** questions

(4 × 7.5 = 30)

11. Explain the construction of a differentiator and an integrator using op-amp.
12. With a neat diagram explain the working of R-2R ladder D/A converter.
13. Explain the fabrication of monolithic IC.
14. Write 8085 instructions in arithmetic and branching groups.
15. Write an assembly language program to multiply two 8-bit numbers.
16. Explain the working of a counter type A/D converter using a neat diagram.

**PART C**

Answer any **FOUR** questions

(4 × 12.5 = 50)

17. Explain the construction and theory of astable multivibrator using op-amp.
18. Explain the construction and working of weighted resistor D/A converter.
19. Explain with neat diagrams how i) a resistor ii) a transistor and iii) a diode is fabricated in an integrated circuit.
20. Draw the block diagram of INTEL 8085 and explain in detail.
21. Write assembly language program using μP 8085 to
  - a) Pick the largest number in an array
  - b) Square root of a perfect square.
22. Write ASM programs in μP 8085 for addition, subtraction and division in direct and indirect mode of addressing.

\$\$\$\$\$\$\$\$