



LOYOLA COLLEGE (AUTONOMOUS), CHENNAI – 600 034

B.Sc. DEGREE EXAMINATION – PHYSICS

THIRD SEMESTER – NOVEMBER 2011

PH 3504/PH 3502 - ELECTRONICS - I

Date : 01-11-2011
Time : 9:00 - 12:00

Dept. No.

Max. : 100 Marks

PART-A

Answer All Questions

(10x2=20 marks)


1. What is a constant current source?
2. State maximum power transfer theorem.
3. What is meant by transistor biasing?
4. State Barkhausen criterion for oscillation.
5. Calculate the CMRR value in decibel of an Op-amp (Given: $A_{CM} = 12$ & $A_{DM} = 8000$).
6. What is a FET?
7. Draw the block diagram of a four – bit parallel binary adder.
8. What is a demultiplexer?
9. What is down counter?
10. What is the difference between synchronous counter and asynchronous counter?

PART-B

Answer ANY FOUR Questions

(4X7.5=30 marks)

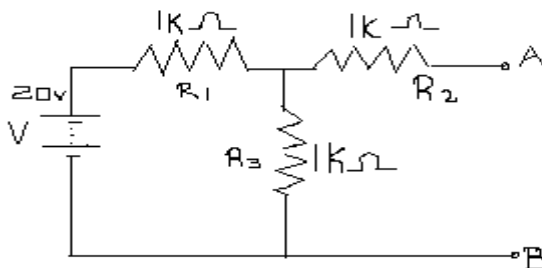11. i) State Thevenin's theorem. (1.5marks)
ii) Find the Thevenin's equivalent circuit for the given circuit. (6 marks)



12. Explain the operation of transistor Bistable multivibrator with a neat diagram.
13. Explain the function of inverting amplifier using Operational amplifier.

14. Simplify using K map $Y=F(A,B,C,D)=\Sigma(0,1,3,5,7,9,11,12,13,14,15)$ and draw a logic circuit for the simplified expression.
15. Explain in detail the working of a 3-bit binary ripple counter.

PART-C

Answer ANY FOUR Questions :

(4x12.5 = 50marks)

16. i) Give the equivalent circuit of a CE amplifier using h- parameters. (3.5 marks)
ii) Derive expression for A_i , A_v and Z_i in terms of h- parameters. (9 marks)
17. Explain the working of transistor RC coupled amplifier with special reference to frequency response, any two advantages and disadvantages.
18. i) Draw the equivalent circuit of a UJT and discuss its working. (6.5 marks)
ii) Draw the V-I Characteristics curve of it and explain. (6 marks)
19. With the help of logic diagram and truth table explain the working of
i) JK flip flop (5 marks)
ii) JK Master slave flip flop (7.5 marks).
20. i) What is shift register? Explain the working of a shift right shift register using JK flip flops. (7.5 marks)
ii) Write short notes on memory devices i) ROM ii) RAM (5 marks)
